

乐清市市政工程建设总指挥部

共射

(1) 电路及晶体管 $2N222$ $\beta=120$

已知: $V_{CC}=+12V$ $R_L=3k\Omega$ $V_i=10mV$ $R_S=600\Omega$

(2) 静态工作点: R_E, R_{B1}, R_{B2}

要求: $|A_v| > 15V/V$ $R_i > 3k\Omega$ $f_L < 50Hz$

取 $I_C = 1mA$

$$\text{取 } V_B = \frac{1}{4} V_{CC} = 3V \Rightarrow R_E = \frac{V_B - V_{BE}}{I_C} = \frac{3-0.7}{1} = 2.3k\Omega$$

当 $I_{R1} \gg I_B$ 时, $V_{BE} \approx V_B = 3V$

$$\Rightarrow 12 \times \frac{R_{B2}}{R_{B1} + R_{B2}} = 3 \Rightarrow R_{B1} = R_{B2} = 3k\Omega$$

① $R_i > 3k\Omega$: 取 $R_{B2} > 3R_i$ 下限 $\Rightarrow$ 取 $R_{B2} = 15k\Omega$ $R_{B1} = 45k\Omega$

② $I_{R_{B1}} \gg I_B$: 取 $I_{R_{B1}} = 10I_B = 0.083mA$ $\Rightarrow$ 取 $R_{B1} = \frac{V_{CC} - V_B}{I_{R_{B1}}} = 108k\Omega$ $R_{B2} = 36k\Omega$

综上, 取标称值 $R_{B2} = 20k\Omega$ $R_{B1} = 60k\Omega$

$\hookrightarrow 36k\Omega$ 固定 + $50k\Omega$ 可调

(3) 动态参数: R_C, R_{E1}

$$\text{取 } I_C = 1mA \Rightarrow r_e = \frac{V_T}{I_C} = 26\Omega$$

$$\text{取 } |A_v| = 20V/V \Rightarrow \frac{R_C \parallel 300\Omega}{26 + R_{E1}} = 20$$

① $R_i > 3k\Omega$: 取 $R_i = 6k\Omega$ $\Rightarrow R_{E1} = 56.6\Omega \Rightarrow R_C = 3.68k\Omega$

$$\Rightarrow R_{E2} = R_E - R_{E1} = 2.243k\Omega$$

② 输出摆幅: 取 $V_C = \frac{2}{3} V_{CC} = 8V \Rightarrow R_C = \frac{V_{CC} - V_C}{I_C} = 4k\Omega \Rightarrow R_{E1} = 60\Omega \Rightarrow R_{E2} = 2.24k\Omega$

综上, 取标称值 $R_C = 3.9k\Omega$ $R_{E1} = 56\Omega$ $R_{E2} = 2.2k\Omega$

(4) 电容 取 $f_L = 40Hz$

$$\Rightarrow C_E = \frac{1}{2\pi f_L [R_{E2} \parallel (R_{E1} + r_e + \frac{R_S \parallel R_{B1} \parallel R_{B2}}{\beta})]} \approx 45\mu F$$

取标称值 $C_E = 47\mu F$ $C_1 = C_2 = 22\mu F$



验算

$$V_{BB} = V_{CC} \frac{R_{B2}}{R_{B1} + R_{B2}}$$

$$R_{BB} = R_{B1} \parallel R_{B2}$$

$$I_E = \frac{V_B - V_{BE}}{R_E + \frac{R_{BB}}{\beta}}$$

$$I_C = \alpha I_E \approx I_{mA} \quad V_C = V_{CC} - I_C R_C > V_B - 0.4$$

$$r_e = \frac{V_T}{I_E}$$

$$A_v = - \frac{R_C \parallel R_L}{r_e + R_{E1}} > 15 \text{ V/V}$$

$$R_{in} = R_{B1} \parallel R_{B2} \parallel [(\beta+1)(r_e + R_{E1})] > 3 \text{ k}\Omega$$

$$R_{out} \approx R_C = 4.3 \text{ k}\Omega$$

$$f_L < 50 \text{ Hz}$$

$$V_{CE} = V_{CC} - I_C R_C - I_E (R_{E1} + R_{E2})$$

$$V_B = \frac{(\beta+1)(r_e + R_{E1})}{(\beta+1)(r_e + R_{E1}) + R_{BB}}$$

$$V_{BE} = V_B - I_E (R_{E1} + R_{E2})$$

当 $R_L = \infty$ 时

$$A_v = - \frac{R_C}{r_e + R_{E1}}$$

实验

$$R_i = \frac{V_i}{V_i - V_o'} \times R$$

$$R_o = \frac{V_o - V_o'}{V_o'} \times R_L$$

反相放大

要求: $R_i \geq 15 \text{ k}\Omega$ $A_v = 15 \text{ V/V}$

$$A_v = - \frac{R_F}{R_1}$$

$$R_i = R_1$$

$$R_o = 0$$

$$\text{取 } R_F = R_1 \parallel R_F$$

反相积分器

$$V_o(t) = - \frac{1}{R_1 C} \int_0^t V_{in}(t) dt$$


$$V_{in}(t) = \begin{cases} 0 & t < 0 \\ E & t > 0 \end{cases} \rightarrow A$$

$$V_{in}(t) = - \frac{E}{R_1 C} t \rightarrow B$$


$$\Rightarrow 2B = \frac{A}{R_1 C} \frac{T}{2}$$

$$C = 0.022 \mu\text{F} \quad \text{取 } R_F \gg \frac{1}{j\omega C} = \frac{1}{2\pi f C} \quad \omega = 2\pi f$$
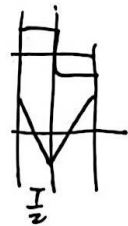
$$\Rightarrow R_F \gg \frac{2B}{\pi A} R_1 \quad \text{取 } R_F > 10 R_1$$



算术运算

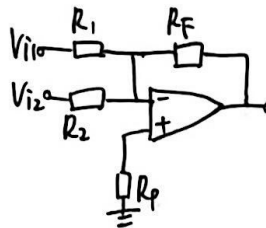

$$\text{取 } R_P = R_1 \parallel R_2 \parallel R_F$$

$$\text{当取 } R_1 = R_2 \quad R_F = R_P \text{ 时} \quad \begin{cases} V_{i2} = + \\ V_{i1} = - \end{cases}$$

$$V_o = \frac{R_F}{R_1} (V_{i2} - V_{i1})$$

否则

$$V_o = \left(\frac{R_P}{R_1 + R_P} \frac{R_1 + R_F}{R_1} V_{i2} - \frac{R_F}{R_1} V_{i1} \right)$$

迟滞比较器

$$V_o = V_{OH} \text{ 时} \quad V_+ = \frac{R_{43}}{R_{43} + R_{44}} (V_{S2} + V_{D1}) + \frac{R_{44}}{R_{43} + R_{44}} V_{42i}$$

$$V_o = V_{OL} \text{ 时} \quad V_+ = - \frac{R_{43}}{R_{43} + R_{44}} (V_{S2} + V_{D2}) + \frac{R_{44}}{R_{43} + R_{44}} V_{42i}$$


当 $V_o = V_{OH}$ 时

$$\text{要使 } \begin{cases} V_{OH} \text{ 时}, V_+ > 0 \Rightarrow V_{42i} > - \frac{R_{43}}{R_{44}} (V_{S2} + V_{D1}) - V_{TH} \\ V_{OL} \text{ 时}, V_+ < 0 \Rightarrow V_{42i} < -V_{TH} \end{cases}$$

当 $V_o = V_{OL}$ 时

$$\text{要使 } \begin{cases} V_{OL} \text{ 时}, V_+ < 0 \Rightarrow V_{42i} < V_{TH} \\ V_{OH} \text{ 时}, V_+ > 0 \Rightarrow V_{42i} > V_{TH} \end{cases}$$

正相

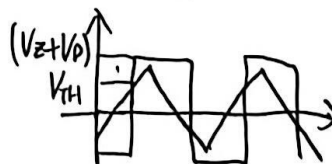

$$V_{TH} = \frac{R_{43}}{R_{44}} (V_{S2} + V_{D1})$$

