
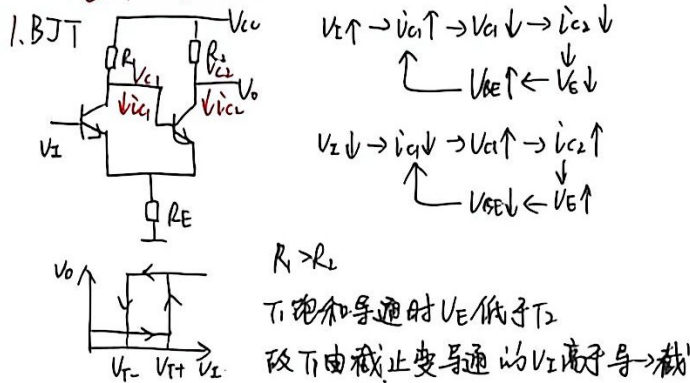


脉冲电路


一、施密特触发器

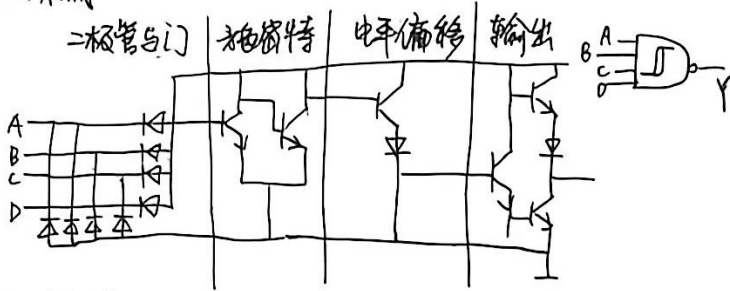


2. 集成...



3. 门电路

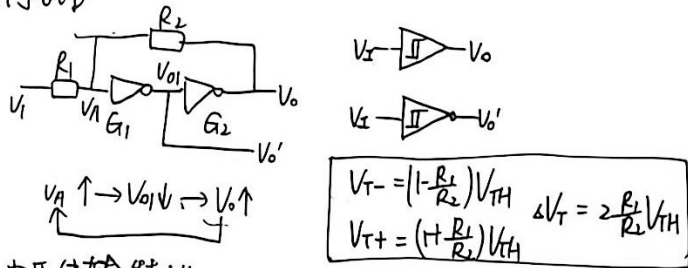


电压传输特性

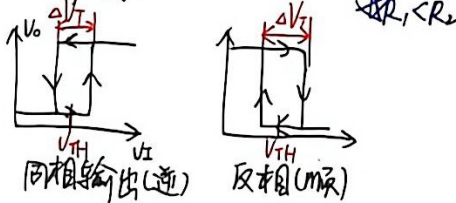


4. 应用

波形变换+脉冲整形+脉冲鉴幅

二、单稳态电路

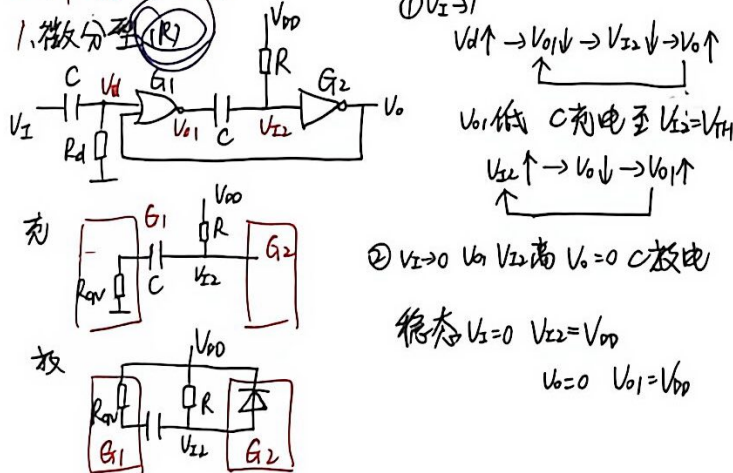


2. 积分型(C)

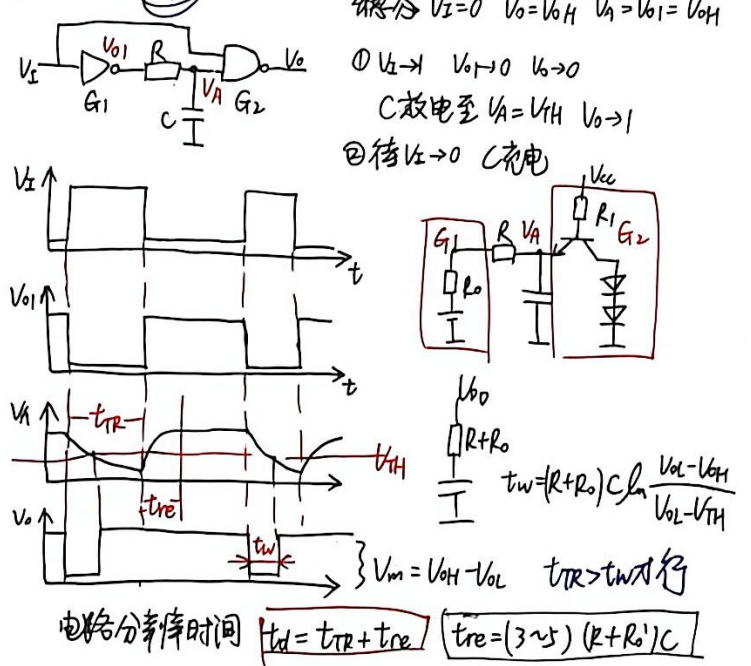

改进:




3. 集成... (74121)

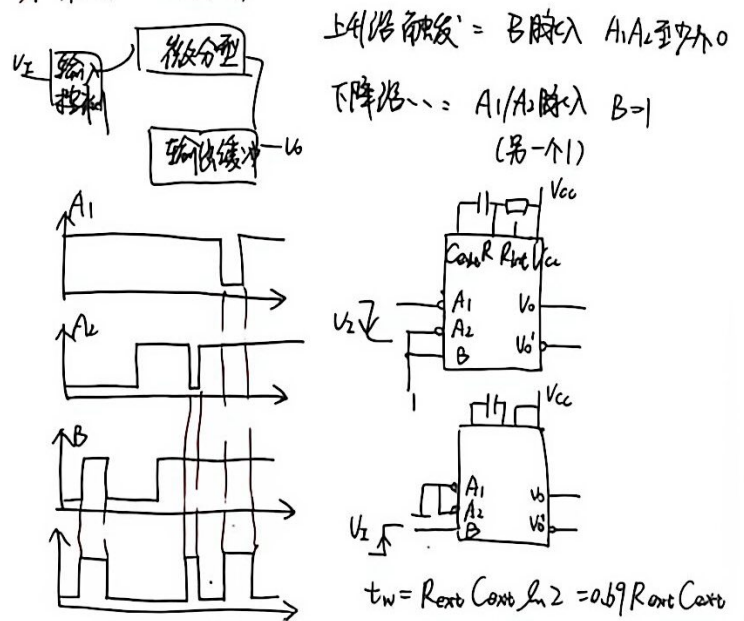

三. 多谐振荡电路

1. 对称式

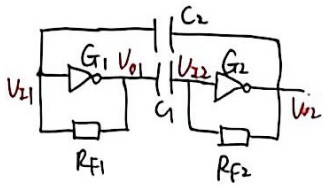

$$R_{E1} = \frac{R_1 R_{F2}}{R_1 + R_{F2}}$$

$$V_{E1} = V_{OH} + \frac{R_{F1}}{R_1 + R_{F2}} (V_{CC} - V_{OH} - V_{BE})$$

C1有两条支路充电更快

V22先上升到VTH

$$V_{OL} \approx 0 \quad V_{C1(0)} = V_{OL}$$



$$V_{C1(\infty)} = V_{E1}$$

$$T_1 = R_{E1} C_1 \ln \frac{V_{E1} - V_{OL}}{V_{E1} - V_{TH}}$$

$$\textcircled{1} V_{E1} \uparrow \rightarrow V_{O1} \downarrow \rightarrow V_{E2} \downarrow \rightarrow V_{O2} \uparrow$$

V22 → 0 V22 → 1 第一个暂稳态

C1充电 C2放电

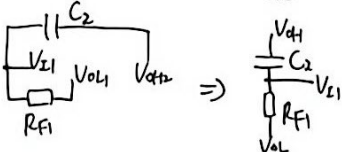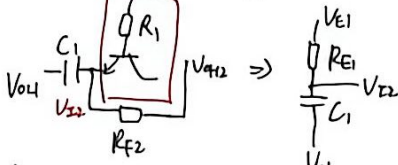


$$\textcircled{2} V_{E2} \uparrow \rightarrow V_{O2} \downarrow \rightarrow V_{E1} \downarrow \rightarrow V_{O1} \uparrow$$

V22 → 0 V22 → 1 第二个暂稳态

C1放电 C2充电
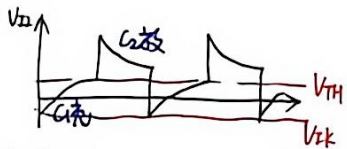
$$\textcircled{3} V_{E1} \text{先上升到 } V_{TH} \Rightarrow \textcircled{1}$$



$$T = 2T_1 = 2R_{E1} C_1 \ln \frac{V_{E1} - V_{OL}}{V_{E1} - V_{TH}}$$


VTH为TTL输入端反向钳位

取V_{OH}=3.4V V_{OL}=0V V_{TH}=1.1V


在R_F << R₁时

$$T \approx 1.3 R_F C$$


2. 非对称式

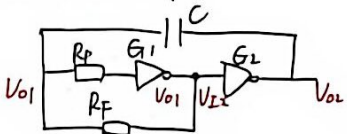

$$R_F \gg R_{ON}$$

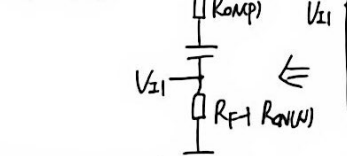

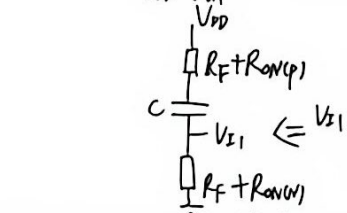
$$T_1 = R_F C \ln \frac{V_{DD} - V_{TH} - V_{OL}}{V_{DD} - V_{TH}} = R_F C \ln \frac{V_{DD} - V_{TH} - V_{OL}}{V_{DD} - V_{TH}}$$



$$T_2 \approx R_F C \ln \frac{0 - (V_{TH} + V_{OL})}{0 - V_{TH}} = R_F C \ln \frac{V_{TH} + V_{OL}}{V_{TH}}$$




$$\textcircled{1} V_{E1} \uparrow \rightarrow V_{E2} \downarrow \rightarrow V_{O2} \uparrow$$

V01 > 0 V01 → 1 第一个暂稳态

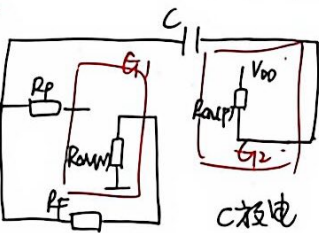

$$\textcircled{2} V_{E2} \uparrow \rightarrow V_{E1} \downarrow \rightarrow V_{O1} \downarrow$$


V01 > 1 V01 → 0

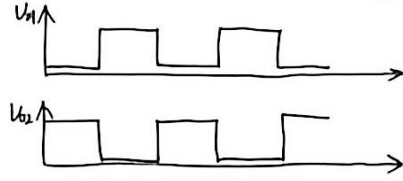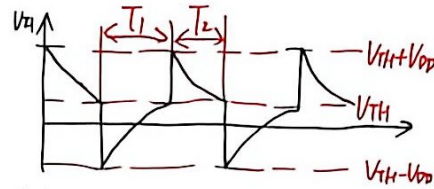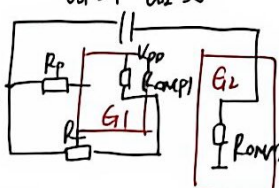

$$T = T_1 + T_2 \approx 2R_F C \ln 2 = 2.2 R_F C$$


3. 环形振荡器

① 最简单

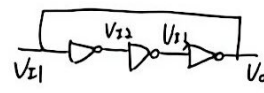





$$T = 2n t_{pd}$$

② 带RC延迟

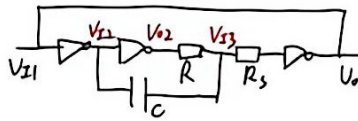

若R₁ >> R₂ >> R V_{OL} ≈ 0



则V_E ≈ V_{OH} R_E ≈ R

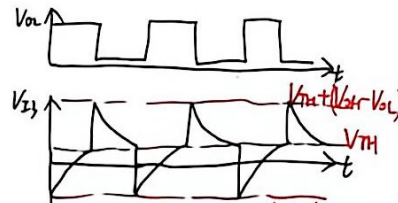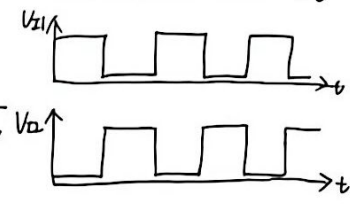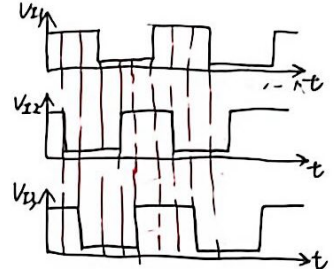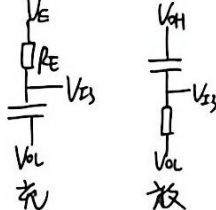

$$T_1 \approx R_C \ln \frac{2(V_{OH} - V_{TH})}{V_{OH} + V_{TH}} \quad T_2 \approx R_C \ln \frac{V_{TH} + V_{OL}}{V_{TH}}$$


$$T = T_1 + T_2 \approx 2.2 R_C$$

4. 施密特构成

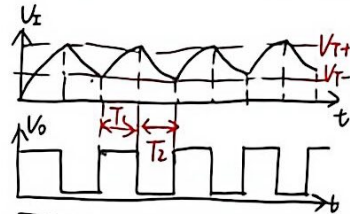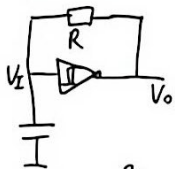

$$T = T_1 + T_2 = R C \ln \frac{V_{OH} - V_T}{V_{OH} - V_{T+}} + R C \ln \frac{V_{T+}}{V_T}$$

5. 石英晶体

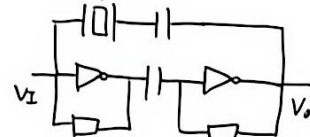

① 工作过程, 波形, 关键电压


② 充放电等效电路

③ 修正关键值, 算充放电时间


图. 555定时器

1. 功能表



R_D'	$U_{I1}(TH)$	$U_{I2}(TR')$	U_O	T_O
0	X	X	低	通
1	$>\frac{2}{3}V_{CC}$	$>\frac{1}{3}V_{CC}$	低	通
1	$<\frac{2}{3}V_{CC}$	$>\frac{1}{3}V_{CC}$	不变	不变
1	$<\frac{2}{3}V_{CC}$	$<\frac{1}{3}V_{CC}$	高	止
1	$>\frac{2}{3}V_{CC}$	$<\frac{1}{3}V_{CC}$	高	止

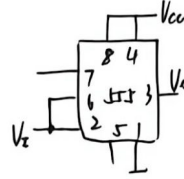

2. 施密特

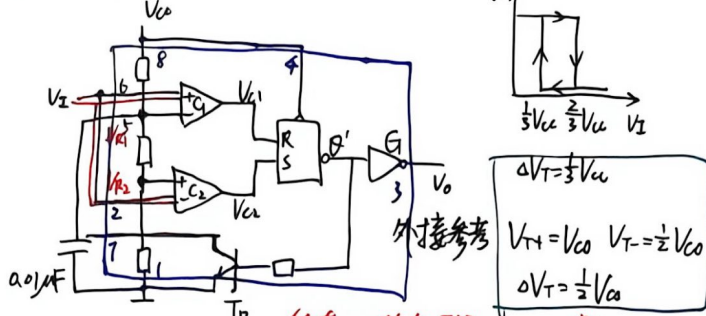

3. 单稳态

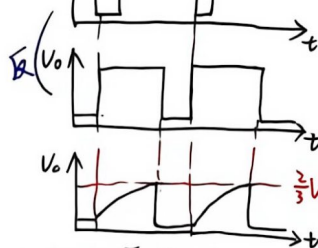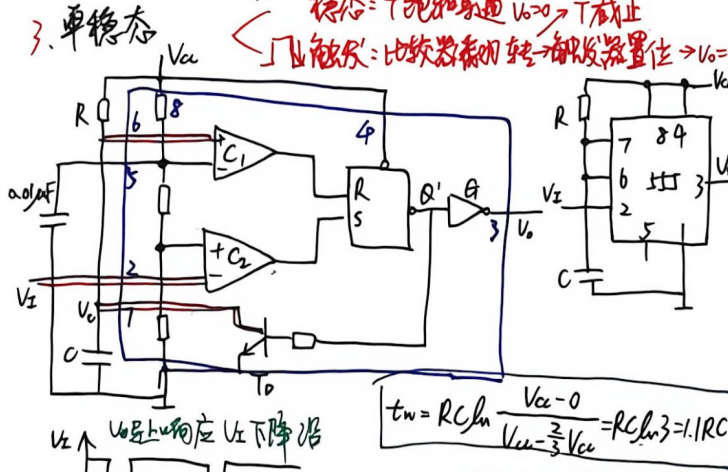

4. 多谐振荡

