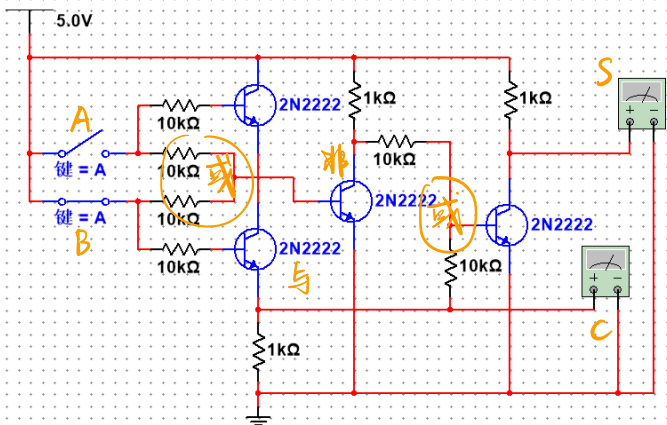



# 半加器



$$0 + 1 + 1 = 1$$

$$x_i \quad y_i \quad c_i \quad c_{i+1}$$

# 全加器

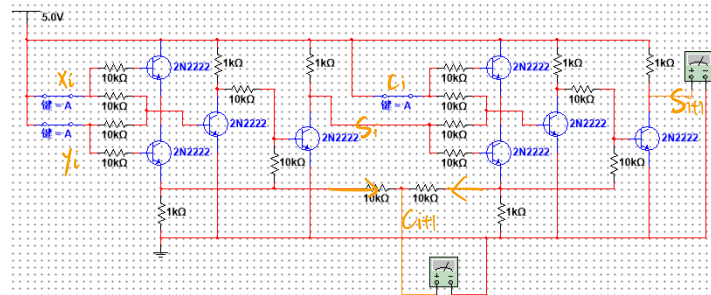

# 4 bit 加法器


$$A = a_3 a_2 a_1 a_0$$

$$B = b_3 b_2 b_1 b_0$$




$$+ \quad + \quad + \quad +$$





$$C_4 \quad C_3 \quad C_2 \quad C_1 \quad S_0$$

# 总电路

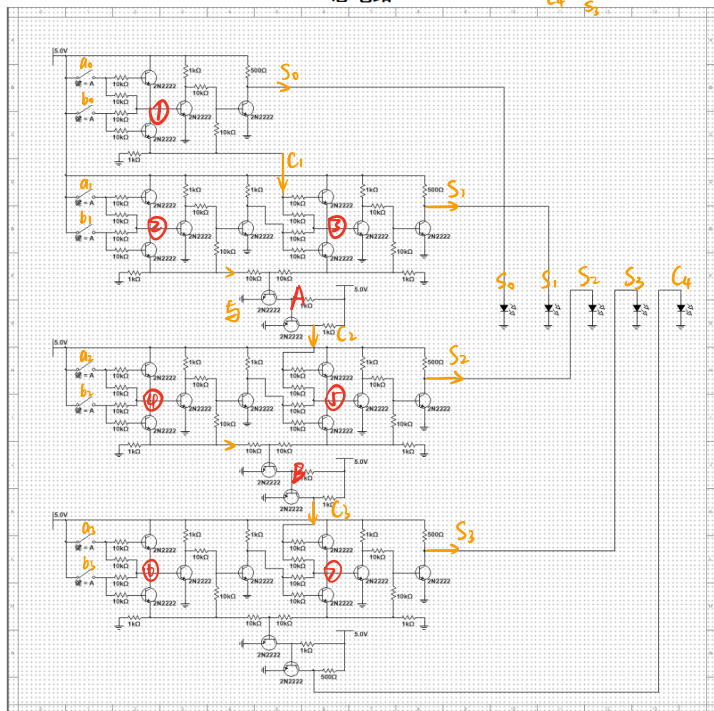

# 3.2 搭建二极管输出电路

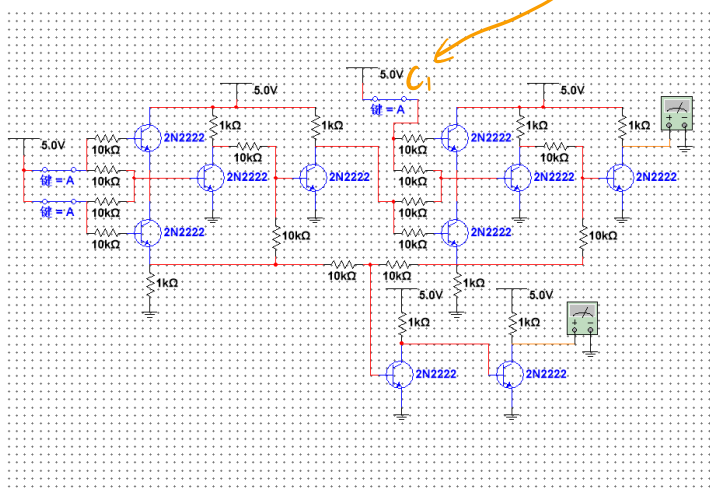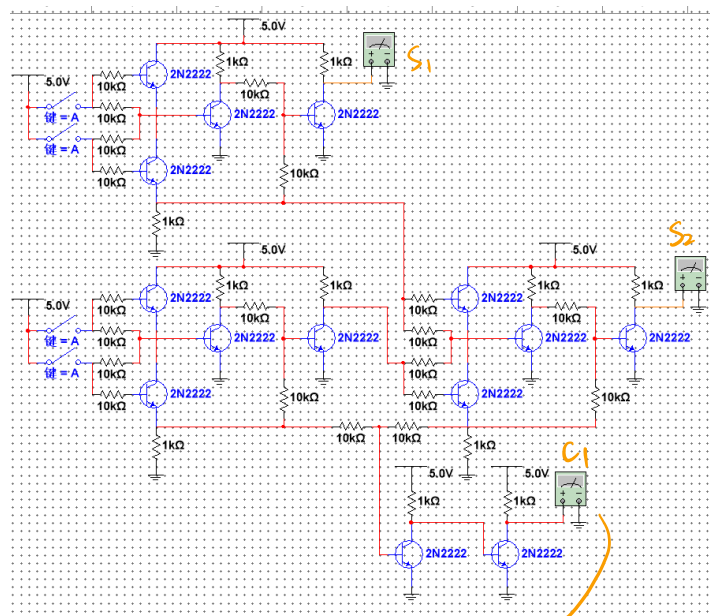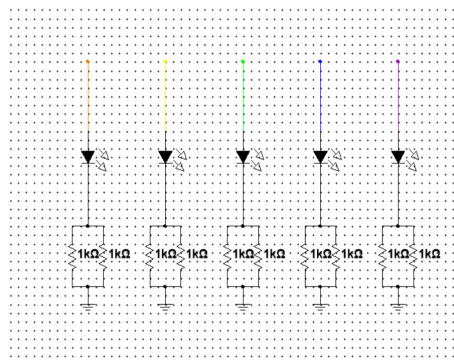

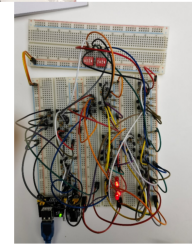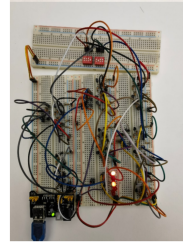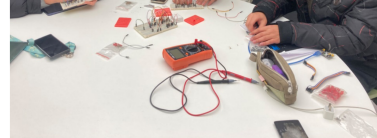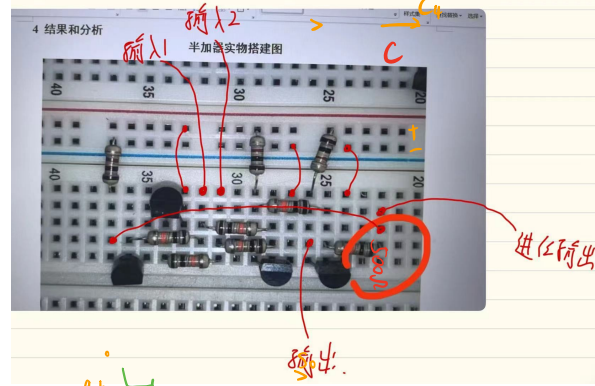

总电路

